

Ohm's Law

Developed for the CSU Physics Van Program by:


**Zak Knott
West Aurora High School
zknott@physicsmonkey.com**

**Dexter Duck
Kelly High School
dduckcps@ameritech.net**


- E. How does adding batteries affect the voltage? How does it affect the current?
- F. How do the current and voltage relate to each other in this experiment?

Graphing Voltage and Current

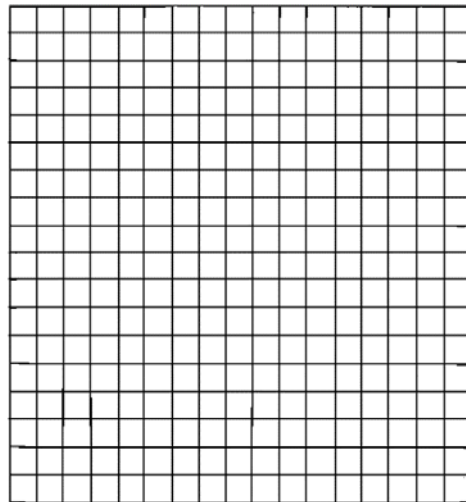- A. Often in science a useful way to analyze data from an experiment is to graph it. In this experiment what was your independent variable? What was your dependant variable?
- B. Create a graph of the data you collected above with your independent variable on the x-axis and your dependant variable on the y-axis.



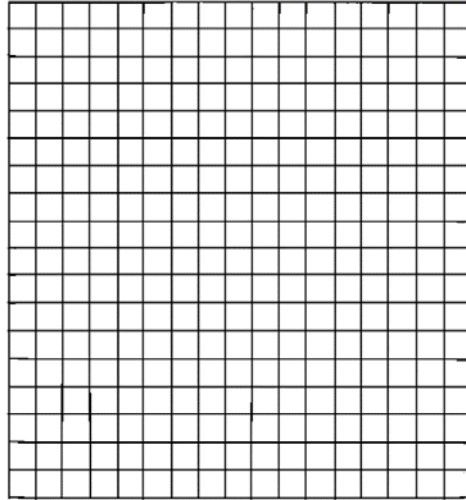- C. What is the slope of your graph? What physical significance does this slope have? (Remember the slope of a position vs. time graph gives velocity. . . is something similar happening here?)
- D. Sometimes it can be useful to look at a graph in a different way. Re-graph your data so that your independent variable is on the y-axis and your dependant variable is on the x-axis.



- E. What is the slope of this new graph?
- F. What physical significance does the slope of this graph have?

Developing a Rule

- A. Use your multimeter to measure the resistance of your resistor. How does this quantity compare to the slope of your graphs above?
- B. For the second graph you created above write out the equation in the graph in slope-intercept formant ($y=mx+b$).

What is the physical significance of your y-intercept (b in the equation). What should the value be (Hint: What is the current when there is zero voltage?)


- C. Using the equation you developed above substitute the variables VOLTAGE, CURRENT, and RESISTANCE into your equation. Once you have finished ask your instructor look at your equation.

Extending the Rule

- A. Repeat the experiment you did above (measuring voltage and current as you add more batteries), however, this time substitute a light bulb for the resistor. Record your data in the table below. *Do not use more than 4 batteries.*

| <i>Number of Batteries</i> | <i>Voltage</i> | <i>Current</i> |
|----------------------------|----------------|----------------|
| | | |
| | | |
| | | |
| | | |

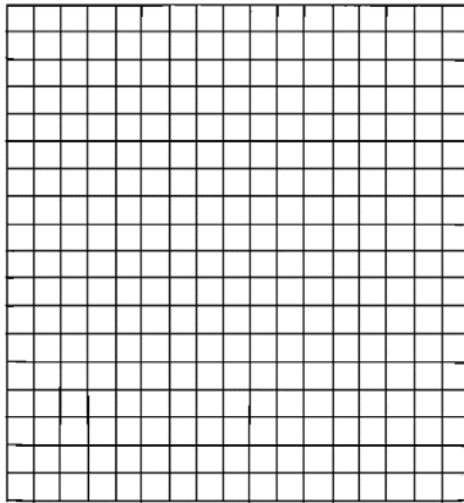- B. Graph the results below, as you saw above voltage should be graphed on the y-axis and current on the x-axis.



- C. This graph is noticeably different from the graph produced by the resistor above. Why is this graph curved?
- D. What does the curve of this graph tell you about the resistance of the light bulb as voltage is increased?

Challenge Questions

- A. What would happen to the current in a circuit if the voltage were doubled (assuming a constant resistance)?

B. What would happen to the current in a circuit if the resistance were halved (assuming a constant voltage)?

C. A 6.2 Volt battery is connected to a 19 Ohm resistor, what current will flow in the circuit?

Equipment

Basic Circuits Kit (includes 2 batteries, 5 alligator clip wires, 5 bulbs , 2 sockets, switch)

Extra Batteries (4-6 additional)

1 Resistor (value must be between 300-800 Ohms)

Multimeter